 


CMPS 375  
Computer Architecture  
Lab 2 (4-bit Adder)  
Combinational Logic: Hierarchical Design

**Lab Objectives**


The purpose of this lab is to build combinational logic circuits and gain increased familiarity with the Nexys4 DDR board. You also learn how to create more complex circuits using a hierarchical design approach.



**Xilinx Nexys4 DDR Board: Artix-7 FPGA (XC7A100TCSG324-1)**
 
## Problem Description

You are required to create a 4-bit adder in VHDL language. The logic diagram of the ripple-carry adder is shown in the textbook. The hierarchical design of the 4-bit adder can be automatically imported from a 1-bit adder in the previous lab. You need to demonstrate addition for the 4-bit adder using the slide switches as the inputs, LED and 7-segment displays as the outputs on the Nexys4 DDR board.



The Logic Diagram for a Ripple-Carry Adder

## Lab Submission

- Check the following 6 files under DispAdder4 sub-folders before your submission
  1. **DispAdder4.vhd**: Display 4-bit adder, design file
  2. **DispAdder4\_tb.vhd**: Display 4-bit adder, test bench
  3. **DispAdder4.xdc**: Display 4-bit adder, constraints file
  4. **Bin2Hex.vhd**: 4-bit binary inputs to 7-segment hex display
  5. **Adder4.vhd**: 4-bit full adder, design file
  6. **Adder1.vhd**: 1-bit adder, design file
- Zip the entire DispAdder4 folder into a single file name: DispAdder4.zip
- Submit **DispAdder4.zip** to Moodle as your lab2.

## Lab Exercise

1. Create a project name, **DispAdder4**. Assign the device to Artix-7 FPGA **XC7A100TCSG324-1**
2. Copy **Adder1.vhd** from Lab1 into this project.
  - In the *Project Manager* tasks of the *Flow Navigator* pane, click the *Add Sources*, select *Add or create design source*, then select **Adder1.vhd**.
3. Create **Adder4.vhd** and complete the following VHDL code.
  - In the *Project Manager* tasks of the *Flow Navigator* pane, click the *Add Sources*, select *Add or create design sources*, then *Create File*.
  - You may get help from “**Generate Statements**” in the VHDL Cookbook. You write VHDL code like GENERATE ... PORT MAP ...

```


LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY Adder4 IS
    GENERIC(CONSTANT N:    INTEGER := 4);
    PORT(
        a:    IN  STD_LOGIC_VECTOR(N-1 DOWNT0 0);    -- Input  a[3..0]
        b:    IN  STD_LOGIC_VECTOR(N-1 DOWNT0 0);    -- Input  b[3..0]
        cOut: OUT STD_LOGIC;                          -- Output cOut
        sum:  OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0)      -- Output sum[3..0]
    );
END Adder4;

ARCHITECTURE behavioral OF Adder4 IS
    COMPONENT Adder1
        PORT(
            a, b, cIn : IN  STD_LOGIC;
            cOut, sum : OUT STD_LOGIC);
        END COMPONENT;
    SIGNAL carry_sig: STD_LOGIC_VECTOR(N DOWNT0 0);
BEGIN
    -- Write Your Code Here
END behavioral;


```

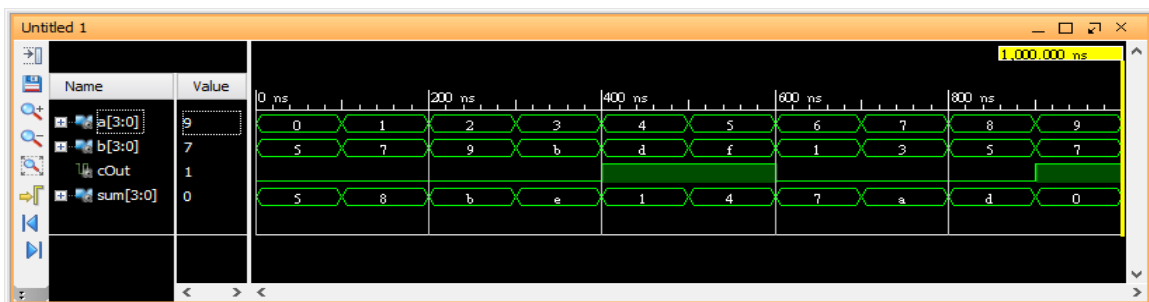4. Create a simulation file `Adder4_tb.vhd` after no compilation errors. Simulate your design: the results are like this figure (Simulation Time: 1000 ns; wait for 100 ns).
  - In the *Project Manager* tasks of the *Flow Navigator* pane, click the *Simulation*, *Run Simulation*, and then *Run Behavioral Simulation*



 5. Create a VHDL file **Bin2Hex.vhd**. Enter and then complete the following VHDL code.

- It displays hexadecimal value (4-bit inputs to a 7-segment display): 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, b (the same as 8 if upper case B), C, d (the same as 0 if upper case D), E, and F
- Position and index of each segment in a 7-segment display hex[6..0] as follows:



- You may help from “Selected Signal Assignment” in the VHDL Cookbook. You write VHDL code like WITH ... SELECT .... WHEN.


```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY Bin2Hex IS
    PORT(
        bin:  IN  STD_LOGIC_VECTOR(3 DOWNTO 0);    -- 4-bit binary inputs
        hex:  OUT STD_LOGIC_VECTOR(6 DOWNTO 0)      -- 7-segment hex display
    );
END Bin2Hex;

ARCHITECTURE behavioral OF Bin2Hex IS
BEGIN
    -- Write Your Code Here
END behavioral;
```

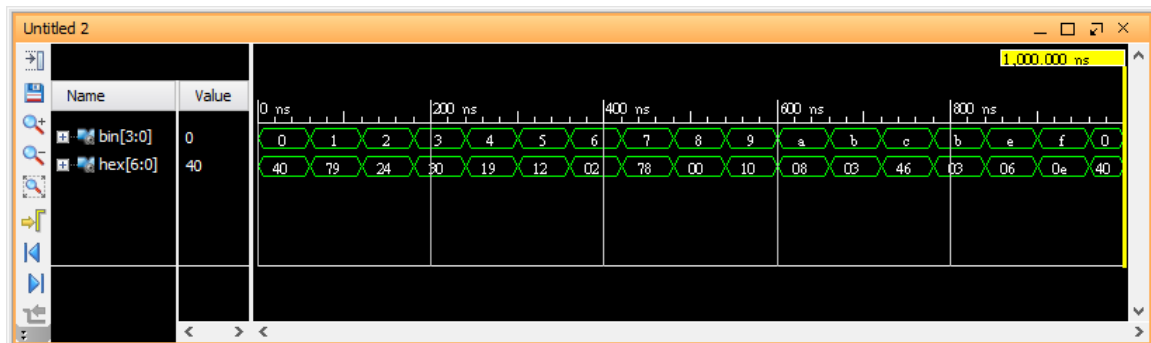6. Create a simulation file Bin2Hex\_tb.vhd after no compilation errors. Simulate your design: the results are like this figure (Simulation Time: 1000 ns; wait for 60 ns).

- In the *Project Manager* tasks of the *Flow Navigator* pane, click the *Simulation*, *Run Simulation*, and then *Run Behavioral Simulation*



7. Create a VHDL file named **DispAdder4.vhd**. Enter and then complete the following VHDL code.

- Note: You need “PORT MAP”

```


LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY DispAdder4 IS
    PORT(
        a:    IN  STD_LOGIC_VECTOR(3 DOWNTO 0);    -- Input  SW[7..4]: a[3..0]
        b:    IN  STD_LOGIC_VECTOR(3 DOWNTO 0);    -- Input  SW[3..0]: b[3..0]
        led:   OUT STD_LOGIC;                       -- Output LED[16]: cOut
        an:    OUT STD_LOGIC_VECTOR(7 DOWNTO 0);    -- Output AN[7..0]: '0' enabled
        hex:   OUT STD_LOGIC_VECTOR(6 DOWNTO 0)    -- Output HEX[6..0]: sum[3..0]
    );
END DispAdder4;

ARCHITECTURE behavioral OF DispAdder4 IS
    COMPONENT Adder4 --4-bit full adder (Adder4.vhd)
        PORT(
            a: IN  STD_LOGIC_VECTOR(3 DOWNTO 0);
            b: IN  STD_LOGIC_VECTOR(3 DOWNTO 0);
            cOut: OUT STD_LOGIC;
            sum: OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
        );
    END COMPONENT;
    COMPONENT Bin2Hex --4-bit binary inputs to 7-segment hex display (Bin2Hex.vhd)
        PORT(
            bin: IN  STD_LOGIC_VECTOR(3 DOWNTO 0);
            hex: OUT STD_LOGIC_VECTOR(6 DOWNTO 0)
        );
    END COMPONENT;
    SIGNAL carry_sig: STD_LOGIC;
    SIGNAL sum_sig: STD_LOGIC_VECTOR(3 DOWNTO 0);
    SIGNAL hex_sig: STD_LOGIC_VECTOR(6 DOWNTO 0);
BEGIN
    -- Write Your Code Here
END behavioral;

```

 8. Create a simulation file **DispAdder4\_tb.vhd** if no compilation errors. Simulate your design: the results like this figure (Simulation Time: 1000 ns; wait for 100 ns).




9. Copy Nexys4DDR\_Master.xdc from Lab1 into this project and rename to **DispAdder4.xdc**. Edited the port names and assign the FPGA I/O pins.


<i>Scalar Ports</i>	<i>Direction</i>	<i>Package Pin</i>	<i>Name</i>
b[0]	IN	J15	SW[0]
b[1]	IN	L16	SW[1]
b[2]	IN	M13	SW[2]
b[3]	IN	R15	SW[3]
a[0]	IN	R17	SW[4]
a[1]	IN	T18	SW[5]
a[2]	IN	U18	SW[6]
a[3]	IN	R13	SW[7]
led	OUT	R12	LED16_B
an[0]	OUT	J17	AN[0]
an[1]	OUT	J18	AN[1]
an[2]	OUT	T9	AN[2]
an[3]	OUT	J14	AN[3]
an[4]	OUT	P14	AN[4]
an[5]	OUT	T14	AN[5]
an[6]	OUT	K2	AN[6]
an[7]	OUT	U13	AN[7]
hex[0]	OUT	T10	CA
hex[1]	OUT	R10	CB
hex[2]	OUT	K16	CC
hex[3]	OUT	K13	CD
hex[4]	OUT	P15	CE
hex[5]	OUT	T11	CF
hex[6]	OUT	L18	CG

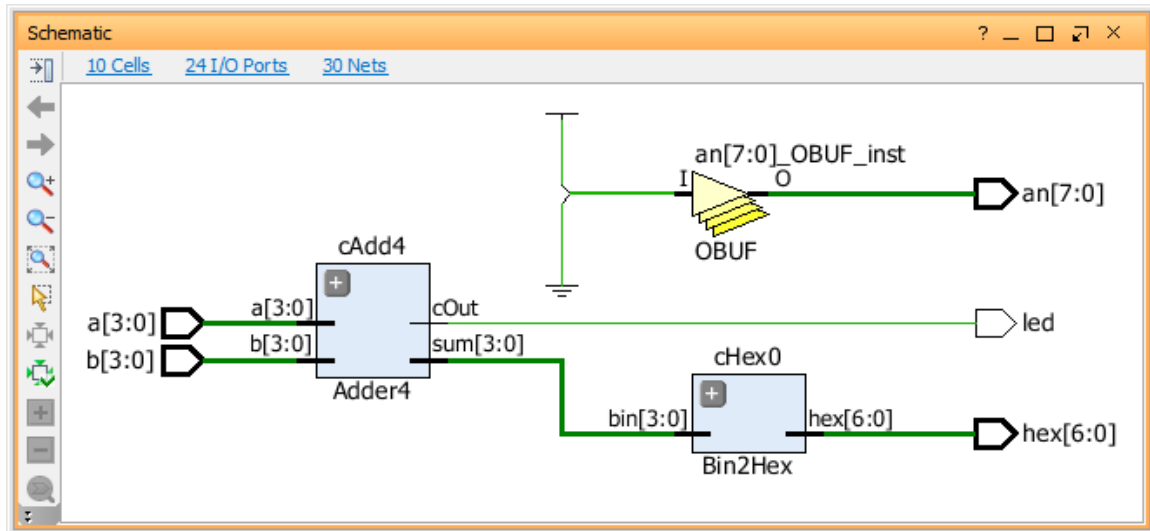10. Synthesize, implement the design, and then generate the bitstream.  
 11. Program and download the design to the FPGA: device choose the download file **DispAdder4.bit**.  
 12. Test and verify functionality of the designed circuit.

- You may get help from schematics: DispAdder4 and Adder4



**DispAdder4 Schematic**

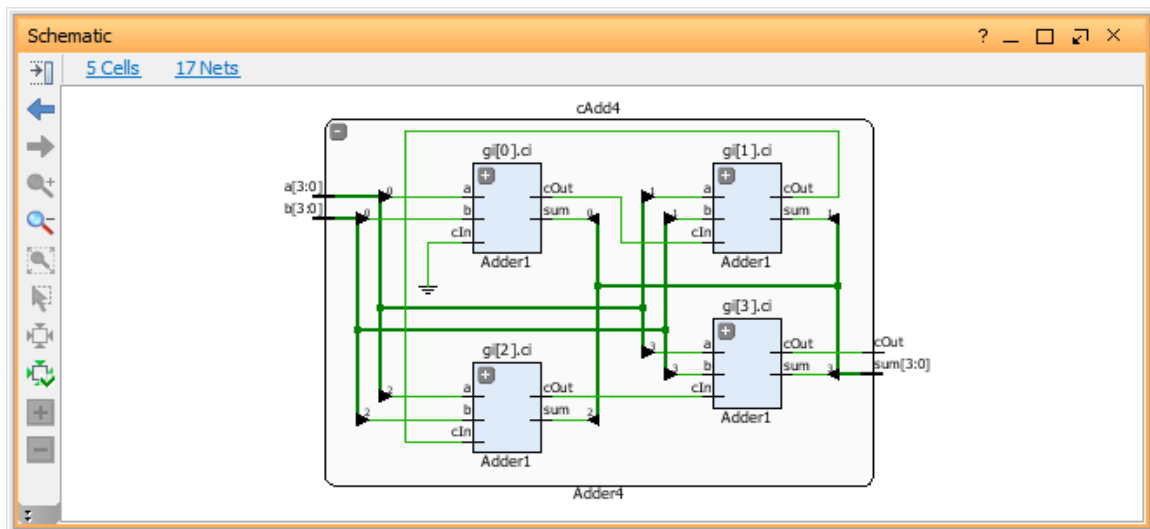

**Adder4 Schematic**